

HALF ADDER & FULL ADDER

Digital Logic Design using Logisim

Half Adder | Full Adder | Truth Tables | Logisim Simulation

KLH-FED-2026-Section-2--Batch-8

[github.com/Keerthan858/KLH-FED-2026-Section-2--Batch-](https://github.com/Keerthan858/KLH-FED-2026-Section-2--Batch-8)

TEAM

Group Members

2620030661

Ande Keerthan

2620030342

Pothuri Nagasai Anirudh Varma

2620030346

Chinthapalli Siri Chandana

2620030347

Saikam Nandhini

2620030428

Wafa Mehajabeen

1. What is a Binary Adder?

A combinational circuit that adds binary numbers.

SUM is the result bit; CARRY is the overflow.

A core building block of ALUs, CPUs and calculators.

Two common circuits: Half Adder and Full Adder.

2. Half Adder

Adds two 1-bit binary inputs: A and B


Half Adder is a simple circuit that adds two single bit binary numbers.

Inputs: A, B

Outputs: Sum (S), Carry (C)

SUM is produced by XOR: $S = A \oplus B$

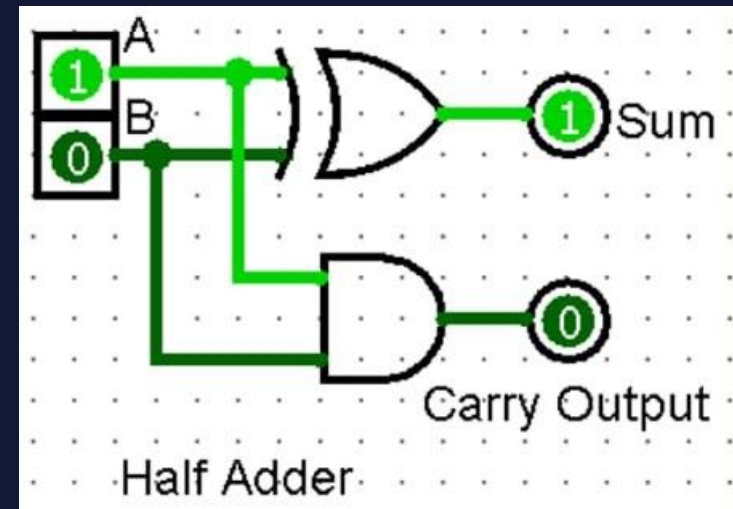
CARRY is produced by AND: $C = A \cdot B$



A	B	SUM ($A \oplus B$)	CARRY ($A \cdot B$)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

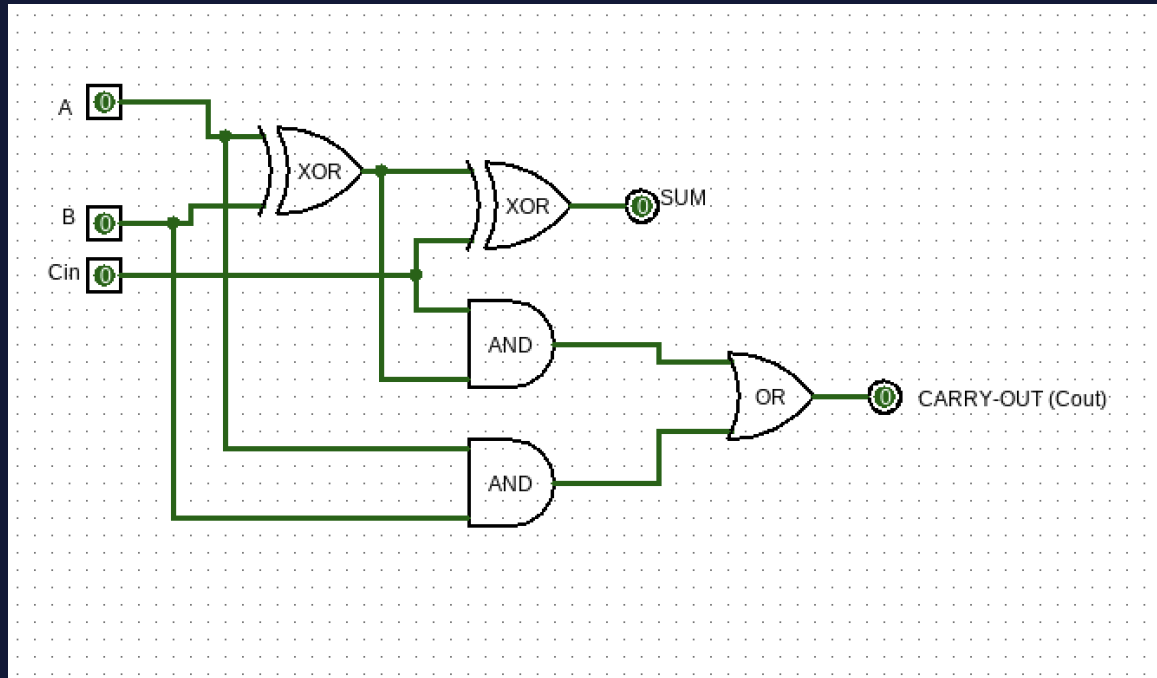3. Full Adder using Two Half Adders

Two Half Adders + one OR gate — modular, easy to build, test and expand



A full Adder is an advanced circuit that adds three single bit binary numbers.

Inputs: A, B, Cin

Outputs: SUM and Carry-Out (Cout)

$$\text{SUM} = A \oplus B \oplus \text{Cin}$$

$$\text{Cout} = AB + \text{Cin}(A \oplus B)$$

Built from two Half Adders + one OR gate.

4. Full Adder Truth Table

A	B	Cin	SUM	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



THANK YOU

Questions?

Half Adder • Full Adder • Logisim